 


Combinational Circuit Design

Combinational Circuit



Design Procedure

1. From the specifications of the circuit, determine the required **number of inputs and outputs** and assign a symbol to each.
2. Derive the **truth table** that defines the required relationship between inputs and outputs.
3. Obtain the **simplified Boolean functions** for each output as a function of the input variables.
4. Draw the **logic diagram** and verify the correctness of the design



Binary Adder

- Half Addder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$

$$C = xy$$

  

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$x \backslash yz$	00	01	11	10
0	m_0	m_1	m_3 1	m_2
1	m_4	m_5 1	m_7 1	m_6 1

$$C = xy + xz + yz$$


$x \backslash yz$	00	01	11	10
0	m_0	m_1 1	m_3	m_2 1
1	m_4 1	m_5	m_7 1	m_6

$$\begin{aligned}
 S &= z \oplus (x \oplus y) \\
 &= z'(xy' + x'y) + z(xy' + x'y)' \\
 &= z'(xy' + x'y) + z(xy + x'y') \\
 &= xy'z' + x'yz' + xyz + x'y'z
 \end{aligned}$$

Full Adder

 


Full Adder using two Half Adder

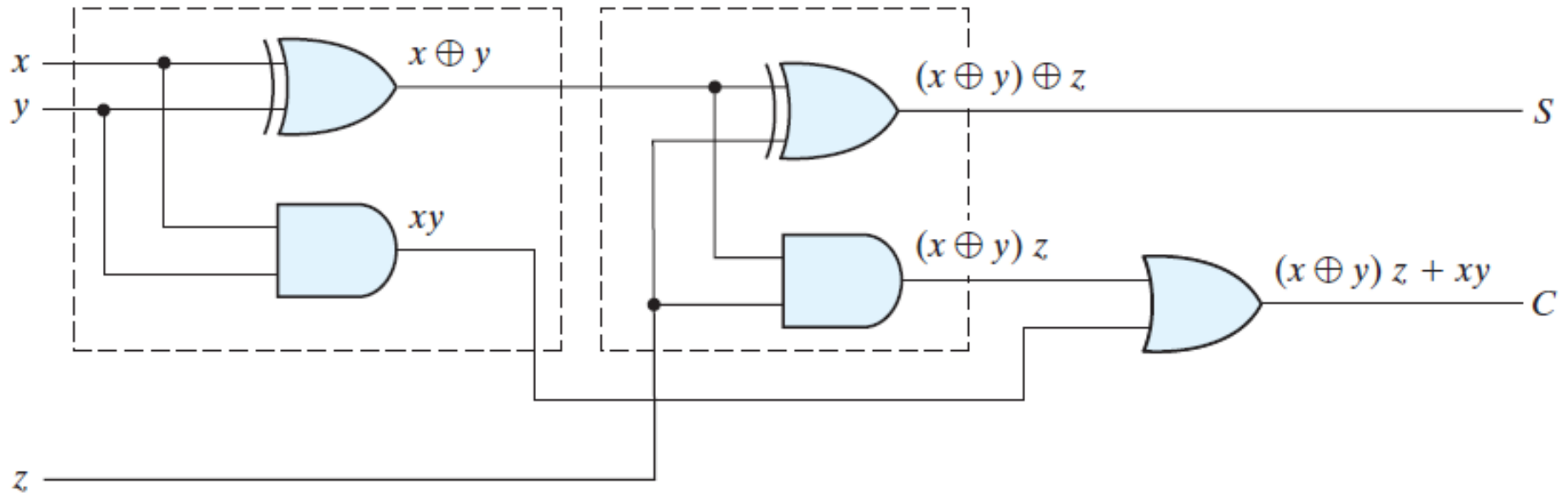

Binary Adder

1011+0011

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

 

Propagation Delay

Carry Look ahead Adder (CLA)

$$A - A_3 A_2 A_1 A_0$$

$$B - B_3 B_2 B_1 B_0$$


$$C_4 \ S_3 \ S_2 \ S_1 \ S_0$$

$$C_o = AB + (A \oplus B)C_i$$

$$C_o = G + PC_i$$

A	B	C _i	C _o
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

CLA

 

$$C_i = G_{i-1} + P_{i-1}C_{i-1}$$



$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_0P_1C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2(G_1 + P_1G_0 + P_0P_1C_0) = G_2 + P_2G_1 + P_1P_2G_0 + P_0P_1P_2C_0$$

$$\begin{aligned} C_4 &= G_3 + P_3C_3 = G_3 + P_3(G_2 + P_2G_1 + P_1P_2G_0 + P_0P_1P_2C_0) \\ &= G_3 + P_3G_2 + P_2P_3G_1 + P_1P_2P_3G_0 + P_0P_1P_2P_3C_0 \end{aligned}$$

CLA Logic

  


Parity Generation and Checking

Even parity Generator

Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$x \backslash yz$				
	00	01	11	10
0	m_0	m_1 1	m_3	m_2 1
1	m_4 1	m_5	m_7 1	m_6


$$P = x \oplus y \oplus z$$

 

Parity Checking

Four Bits Received				Parity Error Check
x	y	z	P	C
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$C = x \oplus y \oplus z \oplus P$$

 

Code Converters

- Convenience
- Security reasons
- Hardware reasons

Examples

- ASCII code
- BCD (Binary coded decimal)
- Excess 3 code
- Gray code

BCD to Excess 3 Converter

b_3	b_2	b_1	b_0	e_3	e_2	e_1	e_0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

$$e_3 = b_3 + b_2b_1 + b_2b_0$$

$$e_2 = \bar{b}_2b_1 + \bar{b}_2b_0 + b_2\bar{b}_1\bar{b}_0$$


$$e_1 = \bar{b}_1\bar{b}_0 + b_1b_0 = b_1 \odot b_0$$

$$e_0 = \bar{b}_0$$

Binary to Gray code


Binary				Gray Code			
b ₃	b ₂	b ₁	b ₀	g ₃	g ₂	g ₁	g ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

Magnitude Comparator

 


Inputs				Outputs		
A_1	A_0	B_1	B_0	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

Decoder

 


Eg. 3 to 8 line decoder

2 to 4 line Decoder

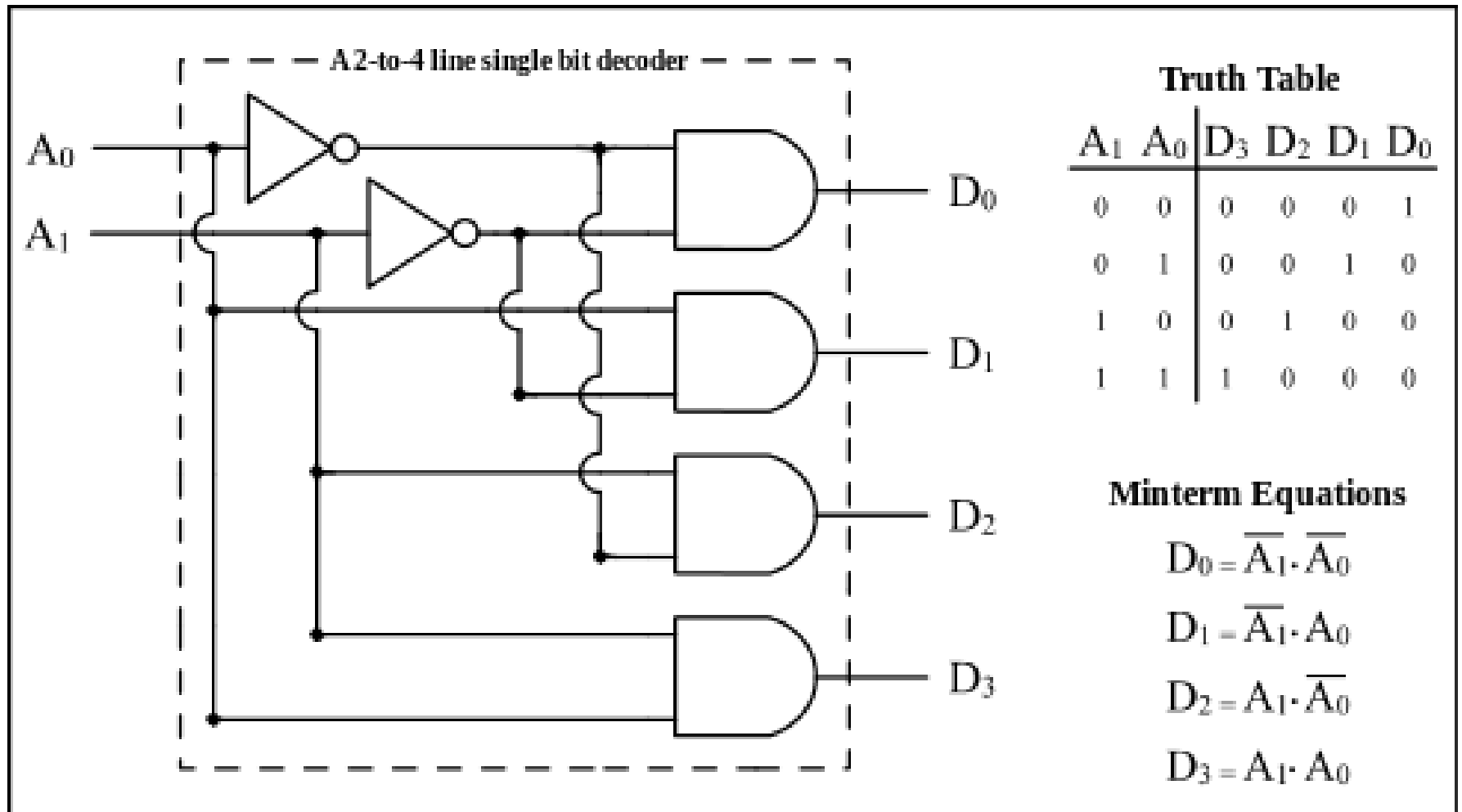

3 to 8 line Decoder

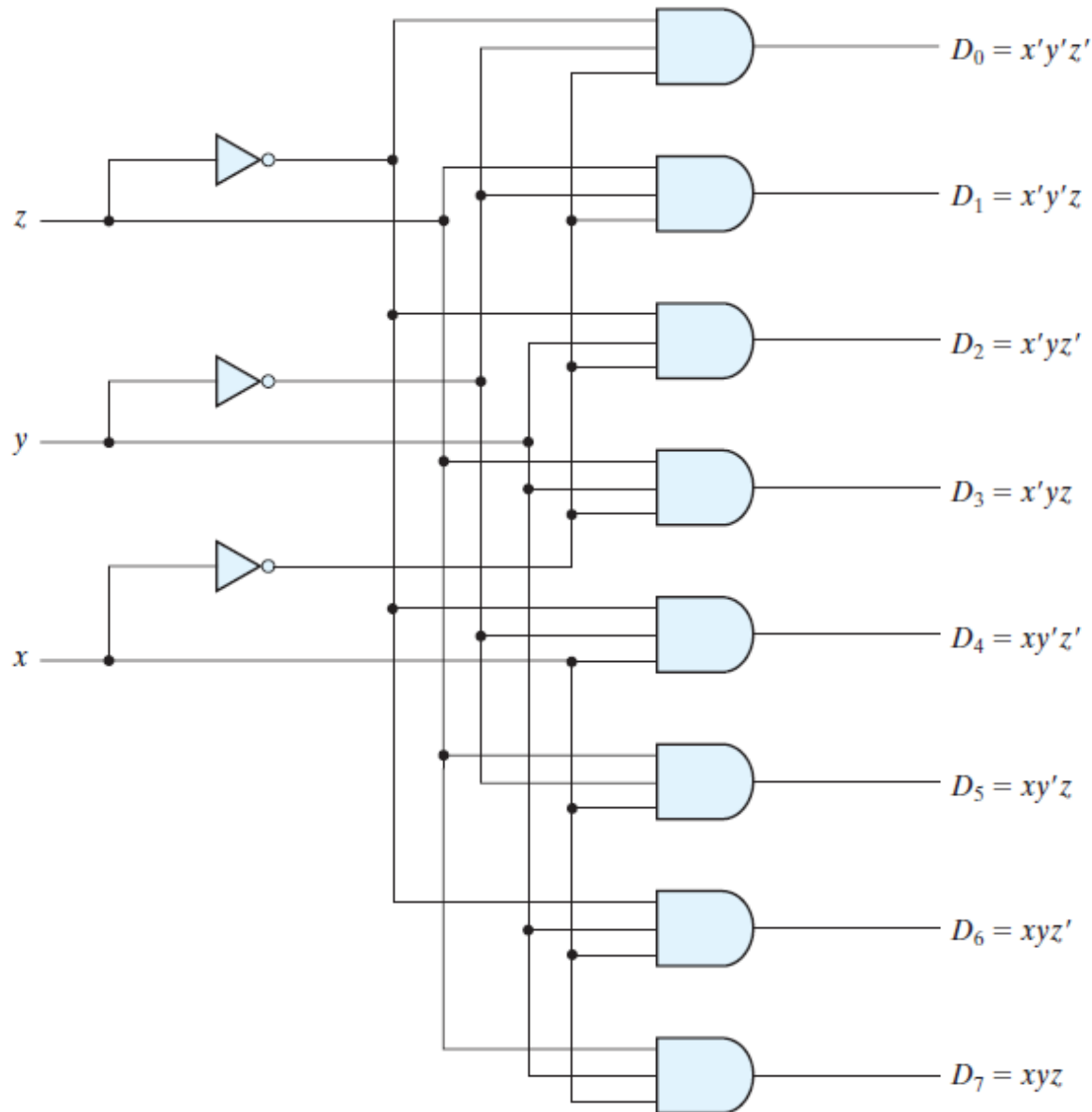


3 to 8 line Decoder

Truth Table

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


Decoder with Enable

- NAND gate based

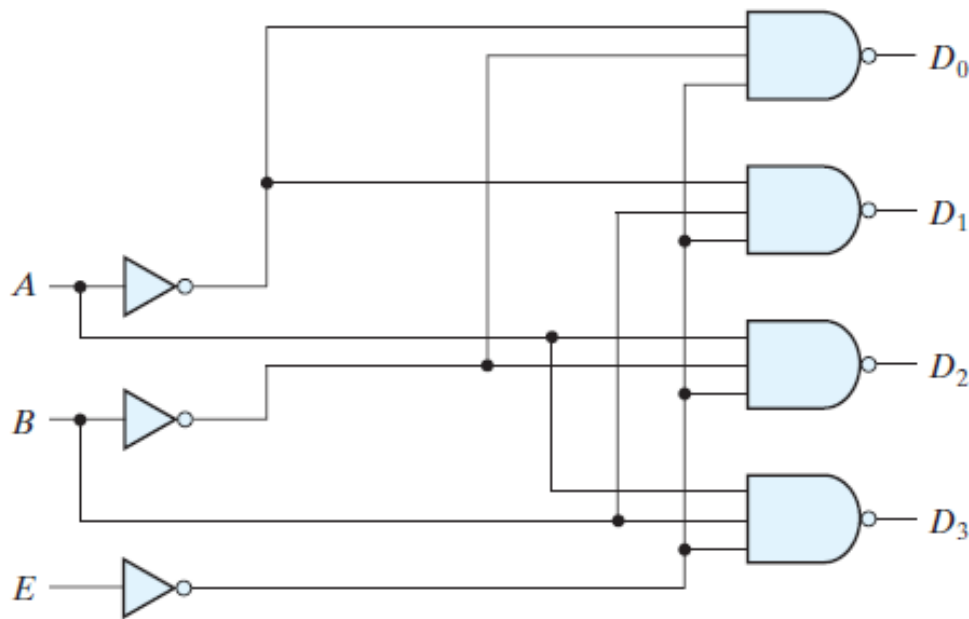

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	1

Connecting Decoders

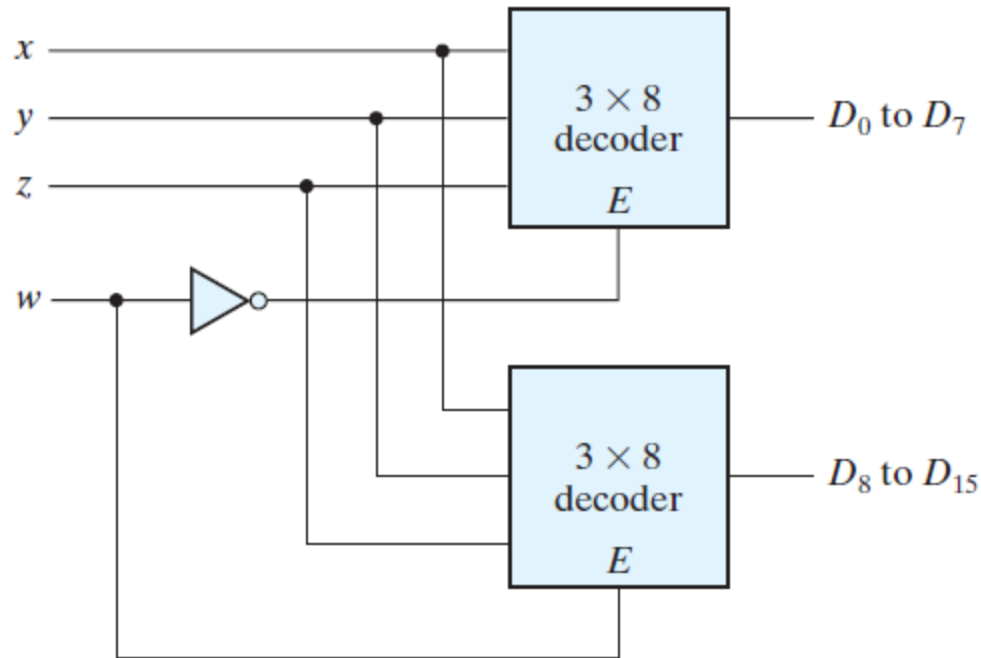

When $w = 0$, top decoder is enabled, bottom decoder is disabled.
Generates output for input 0000 to 0111


When $w = 1$, top decoder is disabled, bottom decoder is enabled.
Generates output for input 1000 to 1111

Combinational Logic Implementation using Decoder

- Full Adder using 3 x 8 Decoder

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

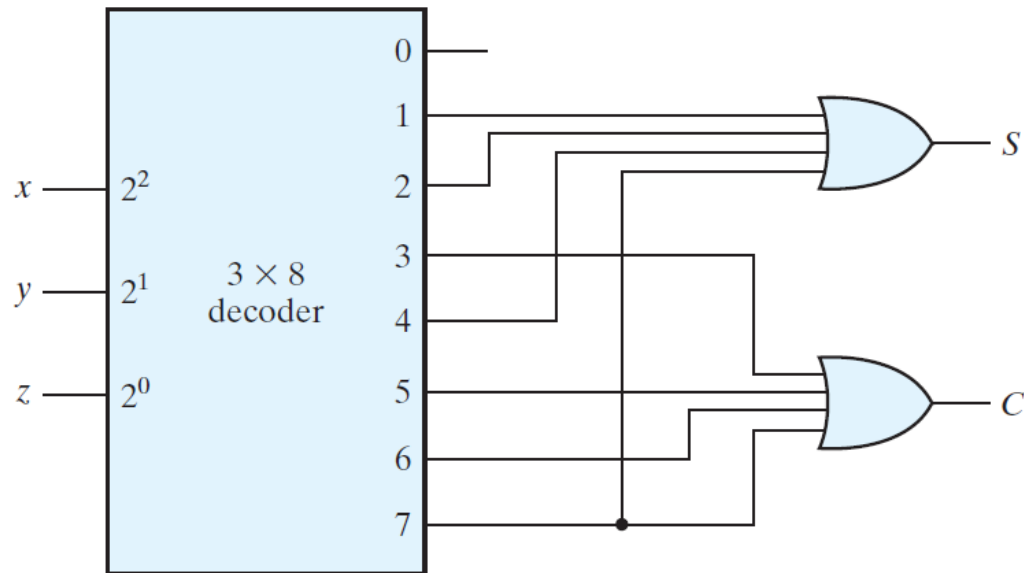

BCD to 7 segment Decoder



- BCD – Binary coded Decimal

Decimal	Binay (BCD)			
	8	4	2	1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1


10 – 00010000

99 – 10011001

100 - 000100000000

  

BCD to 7 segment Decoder

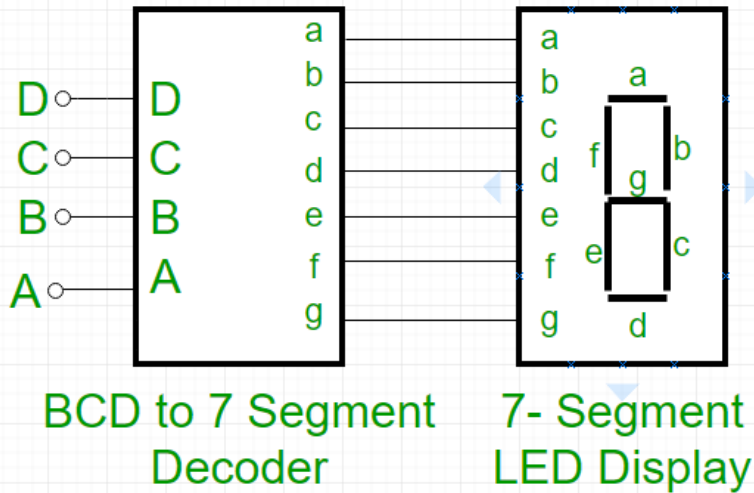

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

K Map for 'a'

AB\CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X


$$a = A + C + AD + \bar{A}\bar{D}$$

K Map for 'b'

AB\CD	00	01	11	10
00	1	1	1	1
01	1	0	1	0
11	X	X	X	X
10	1	1	X	X

$$b = \bar{B} + \bar{C}\bar{D} + CD$$

Encoders

 

Eg. 8 to 3 line encoder

8 to 3 Line Encoder (Octal to Binary Encoder)

Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1



$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$


Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

  


$$\begin{aligned}
 x &= D_2 + D_3 \\
 y &= D_3 + D_1 D'_2 \\
 V &= D_0 + D_1 + D_2 + D_3
 \end{aligned}$$

4 to 2 line priority Encoder

 


Multiplexers

 
- selects binary information from one of many input lines and directs it to a single output line




2 X 1 Multiplexer

 


S	Y
0	I_0
1	I_1

 

4 X 1 Multiplexer

 


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Boolean Function Implementation

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


		z		
		0	1	
xy	00	0	1	$I_0 = z$
	01	1	0	$I_1 = z'$
	11	1	1	$I_3 = 1$
	10	0	0	$I_2 = 0$

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

		CD			
		00	01	11	10
AB	00	m_0	m_1 1	m_3 1	m_2
	01	m_4 1	m_5	m_7	m_6
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8	m_9	m_{11} 1	m_{10}

 


A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

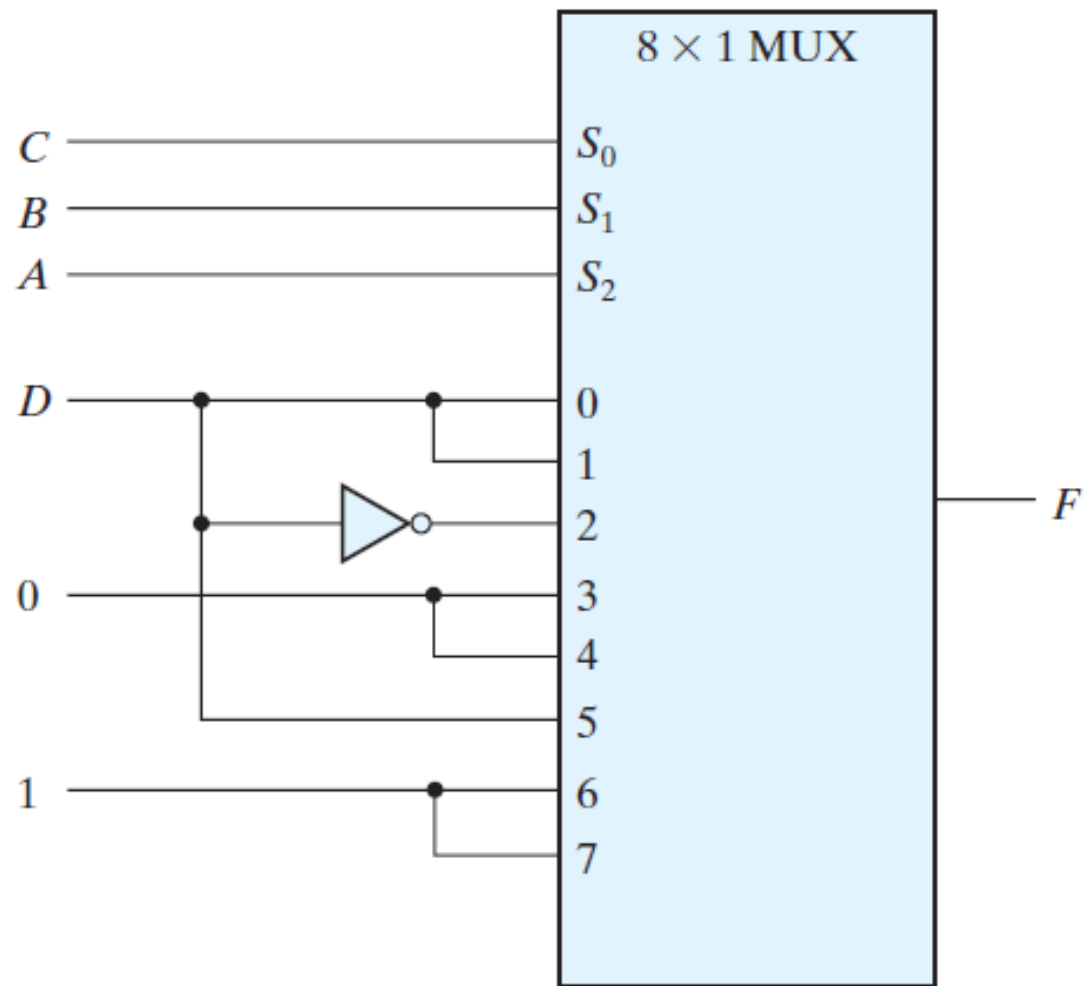


$$F(w, x, y, z) = \sum (1, 4, 5, 7, 9, 12, 13)$$

$wx \backslash yz$					
		00	01	11	10
00	m_0		m_1 1	m_3	m_2
01	m_4 1		m_5 1	m_7 1	m_6
11	m_{12} 1		m_{13} 1	m_{15}	m_{14}
10	m_8		m_9 1	m_{11}	m_{10}


 


Mux Trees

4:1 MUX

 


Three State Gates

  

2X1 Mux using Three state gates

Three State Gates

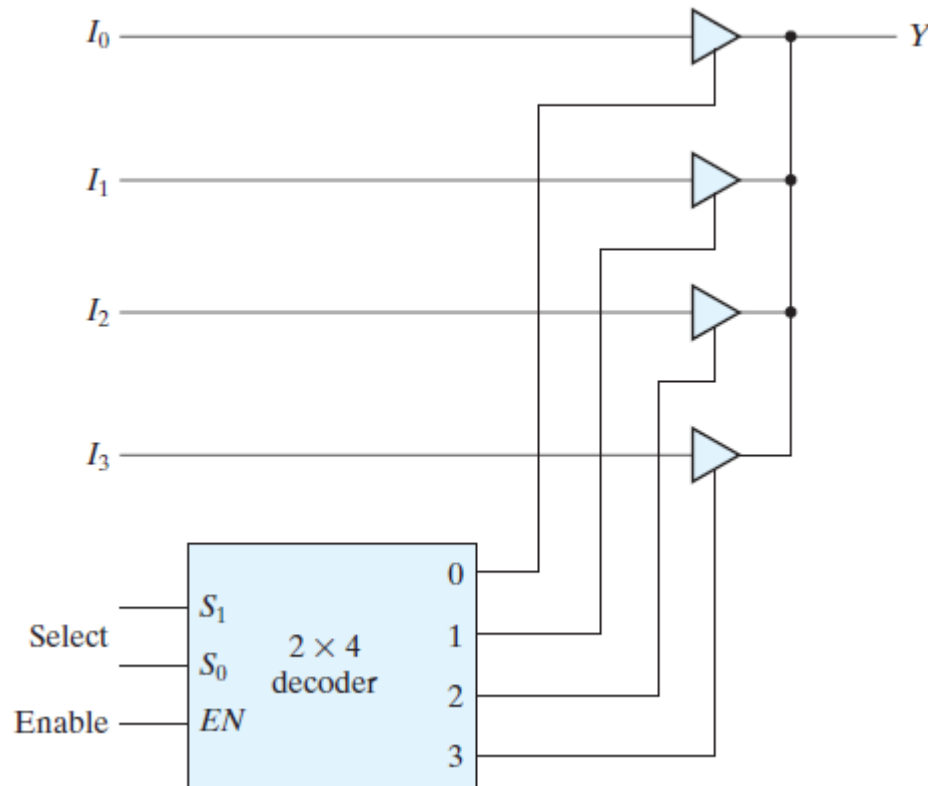

4X1 Mux using Three state gates