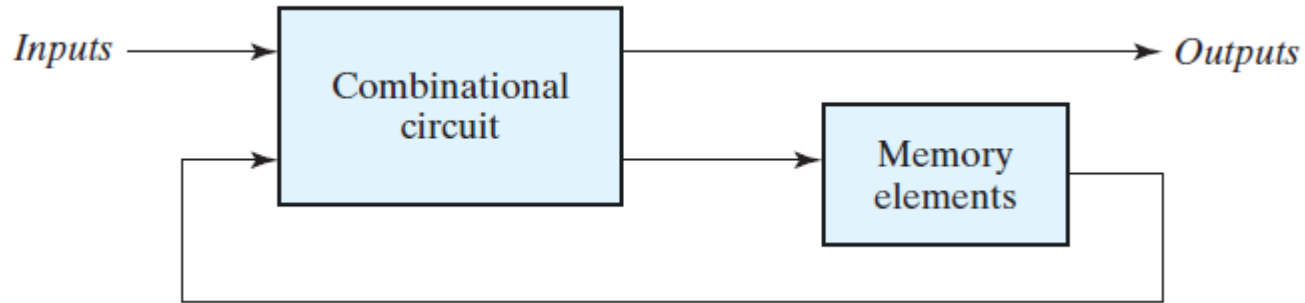



Sequential Circuits

Sequential Circuits



1. Synchronous Sequential Circuit
2. Asynchronous Sequential Circuit

Synchronous Clocked sequential Circuits

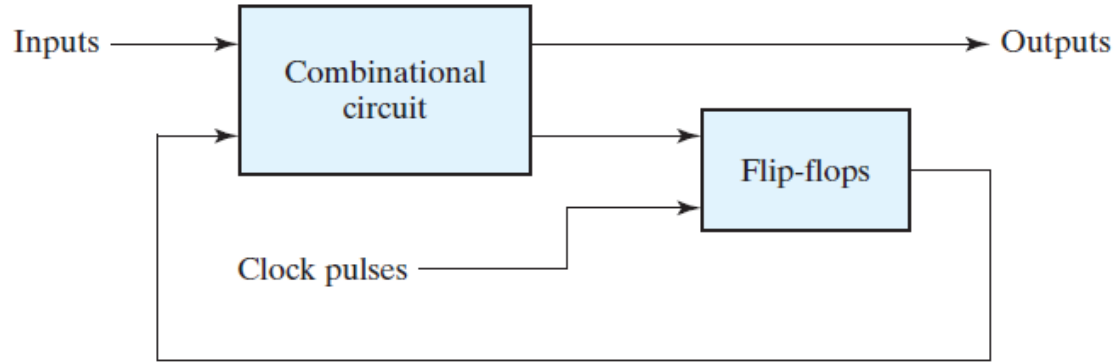

(a) Block diagram




(b) Timing diagram of clock pulses

Storage Elements : Latches


S-R Latch

Logic Circuit

 


Function Table

| S | R | Q | Q' | |
|-----|-----|-----|------|-------------------------|
| 1 | 0 | 1 | 0 | |
| 0 | 0 | 1 | 0 | (after $S = 1, R = 0$) |
| 0 | 1 | 0 | 1 | |
| 0 | 0 | 0 | 1 | (after $S = 0, R = 1$) |
| 1 | 1 | 0 | 0 | (forbidden) |

 

SR Latch (NAND Gate)

 


Logic Circuit

| S | R | Q | Q' |
|-----|-----|-----|---------------------------|
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 (after $S = 1, R = 0$) |
| 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 (after $S = 0, R = 1$) |
| 0 | 0 | 1 | 1 (forbidden) |

Function Table

SR Latch with Control Input

 


Logic Circuit


| En | S | R | Next state of Q |
|------|-----|-----|-----------------------|
| 0 | X | X | No change |
| 1 | 0 | 0 | No change |
| 1 | 0 | 1 | $Q = 0$; reset state |
| 1 | 1 | 0 | $Q = 1$; set state |
| 1 | 1 | 1 | Indeterminate |

Function Table

D Latch

 

Logic Circuit

 

| En | D | Next state of Q |
|------|-----|-----------------------|
| 0 | X | No change |
| 1 | 0 | $Q = 0$; reset state |
| 1 | 1 | $Q = 1$; set state |

Function Table

Clock Response



(a) Response to positive level




(b) Positive-edge response





(c) Negative-edge response


Triggering of Flip-flops

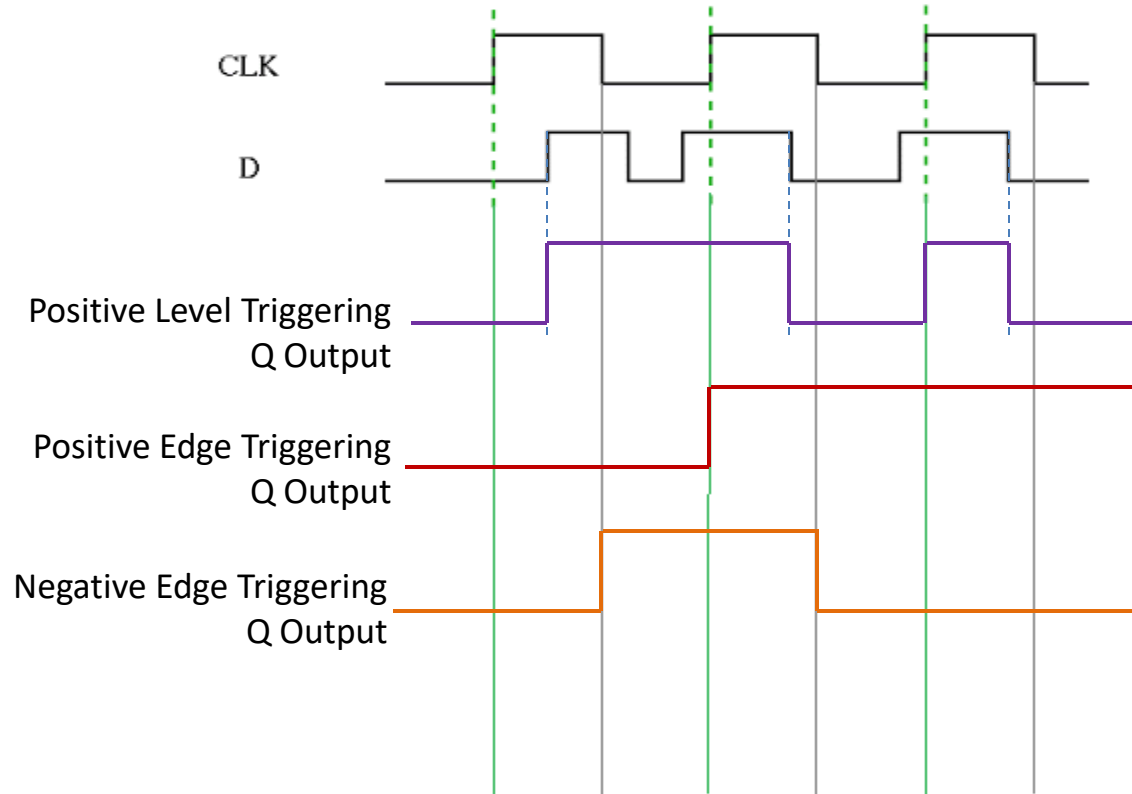

Edge Triggered D Flip-Flop


 
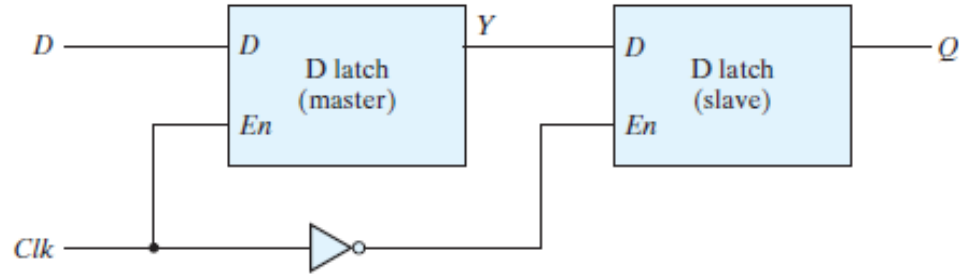


(a) Positive-edge

 

(a) Negative-edge

J-K Flip flop

  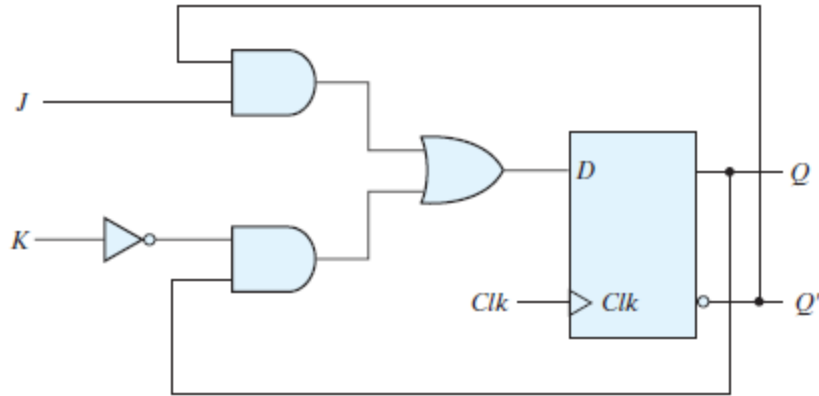


Flip-Flop Characteristic Tables

JK Flip-Flop



| J | K | Q(t + 1) | |
|---|---|----------|------------|
| 0 | 0 | Q(t) | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | Q'(t) | Complement |

T Flip flop

 


T Flip-Flop

| T | $Q(t + 1)$ |
|-----|--------------------|
| 0 | $Q(t)$ No change |
| 1 | $Q'(t)$ Complement |

  


Flip-flops - Summary

 

D Flip-Flop

| D | Q(t + 1) | |
|----------|-----------------|-------|
| 0 | 0 | Reset |
| 1 | 1 | Set |


$$Q(t + 1) = D$$

 

JK Flip-Flop

| J | K | Q(t + 1) | |
|----------|----------|-----------------|------------|
| 0 | 0 | $Q(t)$ | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | $Q'(t)$ | Complement |

$$Q(t + 1) = JQ' + K'Q$$

 

T Flip-Flop


| T | Q(t + 1) | |
|----------|-----------------|------------|
| 0 | $Q(t)$ | No change |
| 1 | $Q'(t)$ | Complement |

$$Q(t + 1) = T \oplus Q$$

$$= TQ' + T'Q$$


Counters

- Ripple Counter
- Synchronous Counter


 


The input that sets the flip-flop to 1 is called ***preset*** or *direct set* .
The input that clears the flip-flop to 0 is called ***clear*** or *direct reset* .

Frequency Divider

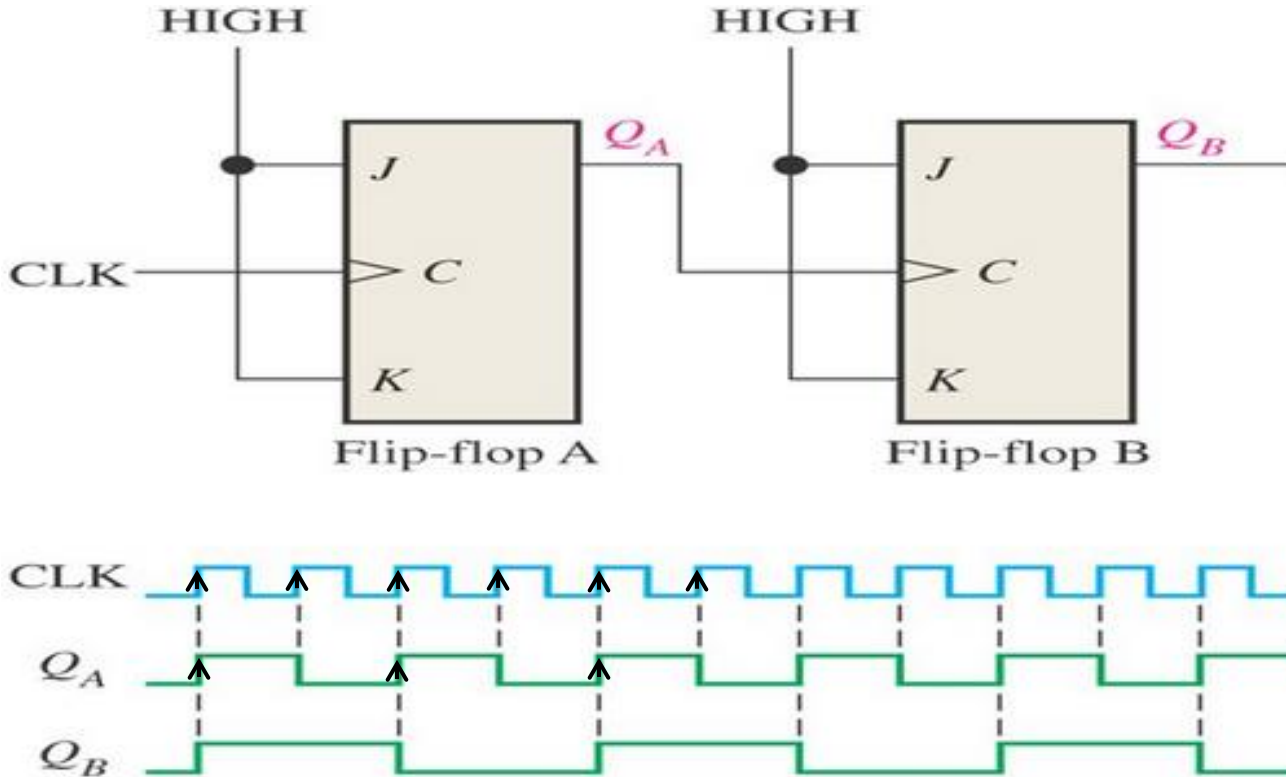

4 bit Binary Ripple Counter

  

| ck | A ₃ | A ₂ | A ₁ | A ₀ |
|----|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 |
| 11 | 1 | 0 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 |
| 14 | 1 | 1 | 1 | 0 |
| 15 | 1 | 1 | 1 | 1 |

0 to $(2^n - 1)$ count using n flip flops – Q output
 $(2^n - 1)$ to 0 count using n flipflops – \bar{Q} output